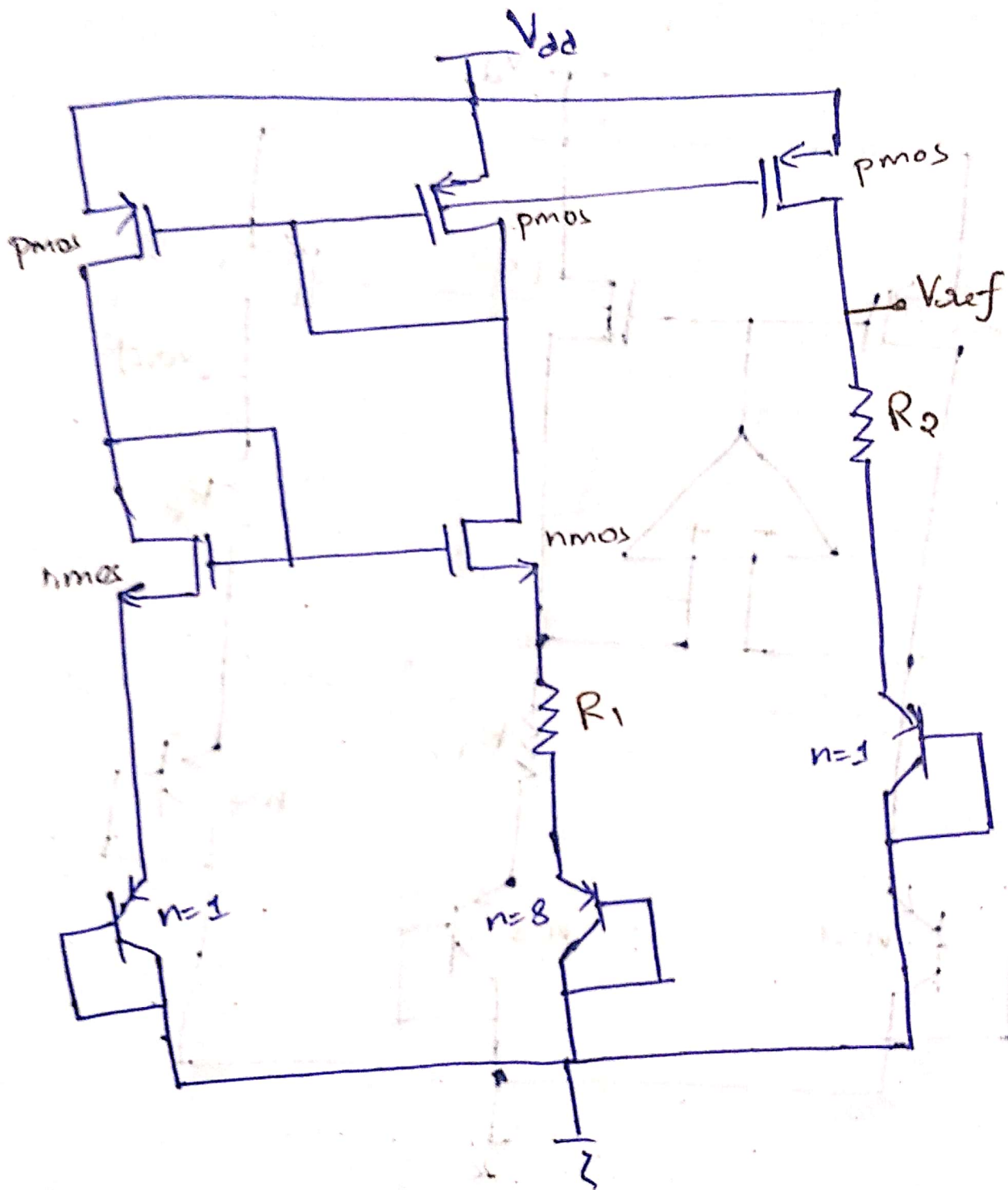


BGR with op-amp:-




BGR with current mirror

Design:-

→ To achieve temperature independence, BGR circuit rely on two temperature-dependent voltage components.

1) PTAT:- This component increases linearly with temperature and is typically derived from the thermal voltage

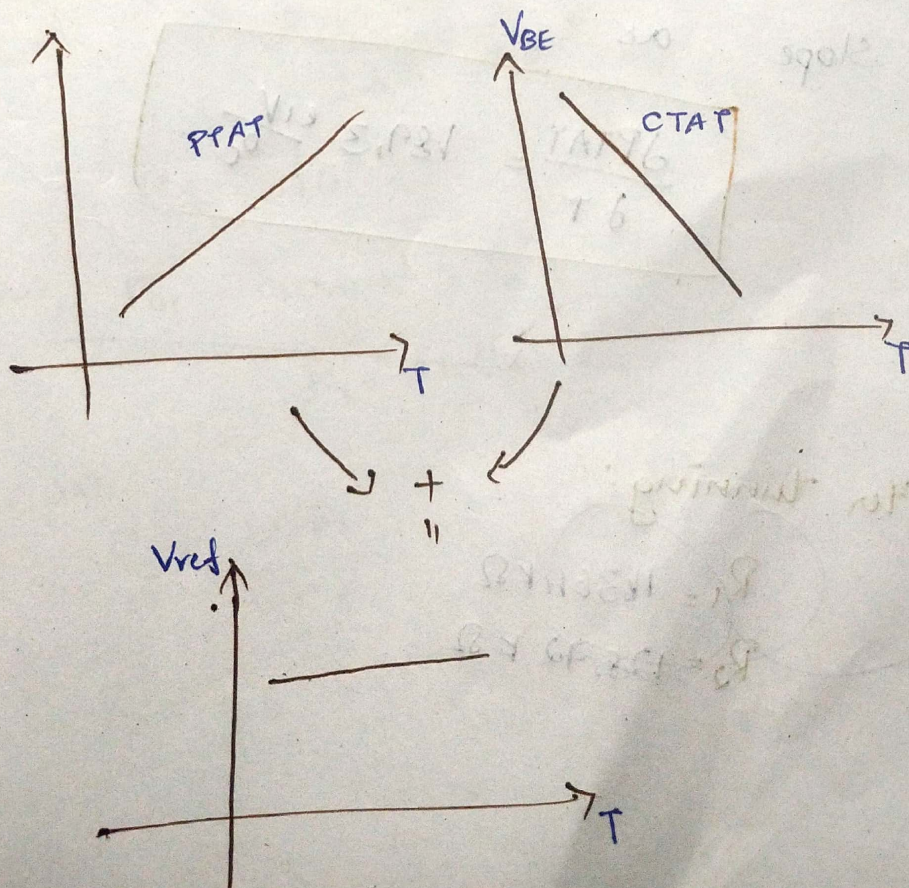2) CTAT:- This component decreases linearly with temperature and is generated using the base-emitter voltage of BJT.



For CTAT slope :-

→ The slope of CTAT is derived from
Simulating test circuit 1

→ we are using 0.180 nm technology

$$\therefore \boxed{\frac{\partial V_{BE}}{\partial T} = -1.938 \frac{mV}{^{\circ}C}}$$

For PTAT slope :-

→ we have taken multiplier, $n=3$

→ For this we have plotted $V_{BE} - V_{BE}^n$
with varying temperature,

→ From this we have found out the
slope as

$$\boxed{\frac{\partial PTAT}{\partial T} = 189.3 \frac{mV}{^{\circ}C}}$$

→ Now we need to adjust PTAT such that it gets cancelled with CTAT using R_1, R_2 .

here

$$V_{out} = \underbrace{\frac{R_2}{R_1} \ln n V_T}_{PTAT} + \underbrace{V_{BE}}_{CTAT}$$

diff w.r.t Temperature.

$$\frac{dV_{out}}{dT} \Rightarrow \frac{d}{dT} \left(\frac{R_2}{R_1} \ln n V_T + V_{BE} \right) = 0$$

$$0 = \alpha_1 \frac{dPTAT}{dT} + \frac{dV_{BE}}{dT}$$

$$\alpha_1 = \frac{-\frac{dV_{BE}}{dT}}{\frac{dPTAT}{dT}}$$

$$= \frac{1.938 \times 10^{-3}}{189.3 \times 10^{-6}}$$

$$\alpha_1 = 10.23$$

now, For current, $I_0 = 5 \mu A$

$$R_1 = 11.364 k\Omega$$

now,

$$R_2 = \frac{\alpha_1 R_1}{\ln 8} = \frac{11.364 \times 10.23}{\ln 8}$$

$$R_2 = 128.72 k\Omega$$

After tuning:-

For current mirror based BGR:-


$$R_1 = 13.22 \text{ k}\Omega$$

$$R_2 = 118.87 \text{ k}\Omega$$

For op-amp based BGR:-

$$R_1 = 11.36 \text{ k}\Omega$$

$$R_2 = 110.9 \text{ k}\Omega$$

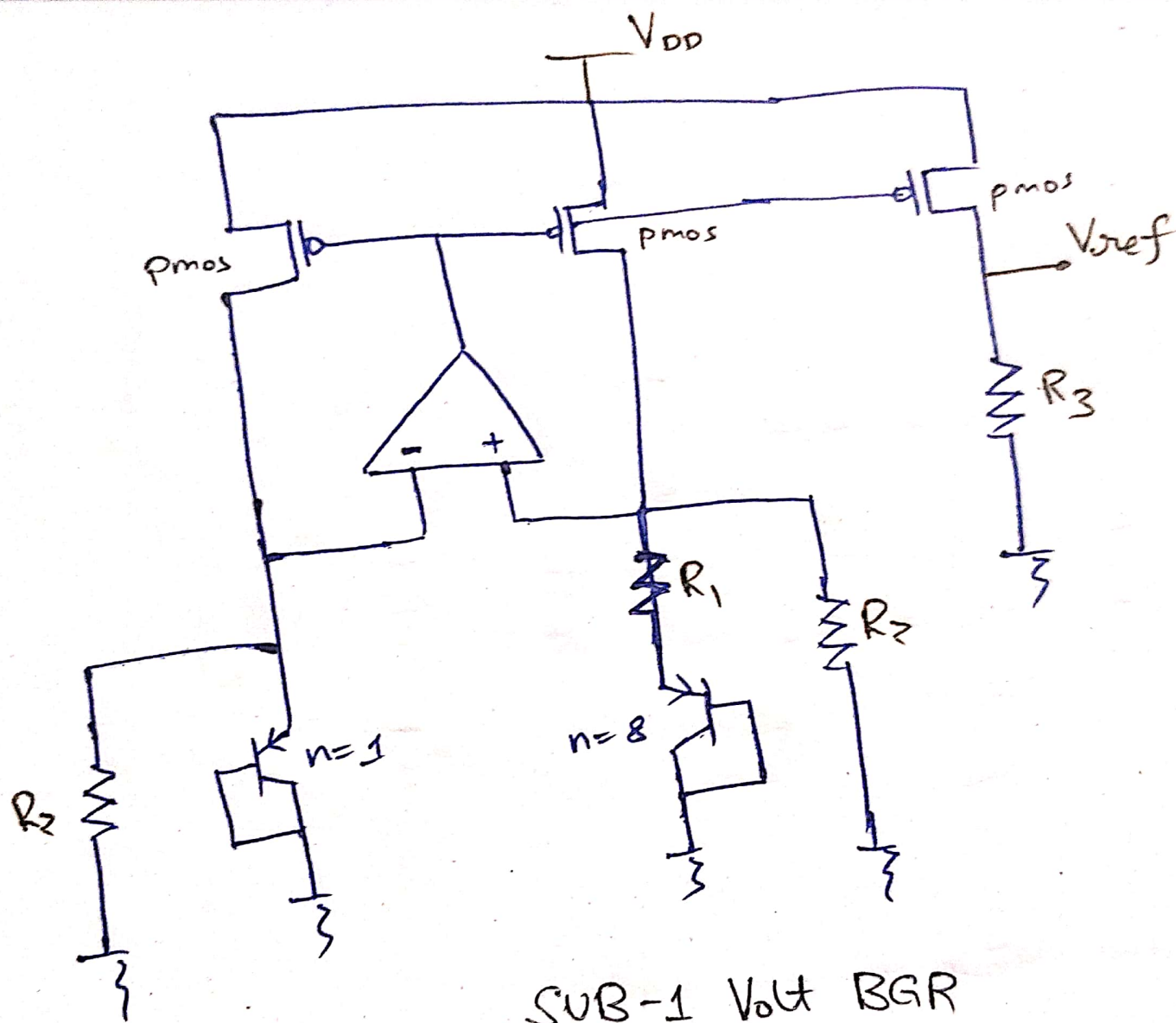

SUB-1 Volt BGR

Design of Sub 1 Volt BGR using op-amp based BGR:-

For normal opamp based BGR

$$V_{out}|_{opamp} = V_{BE} + \frac{R_2}{R_1} V_T \ln(n).$$

For Sub 1 Volt BGR,

$$\begin{aligned} V_{out} &= \frac{R_3}{R_2} \left(V_{BE} + \frac{R_2}{R_1} V_T \ln(n) \right) \\ &= \frac{R_3}{R_2} V_{out}|_{opamp} \end{aligned}$$

For $V_{out} = 0.75V$

$$0.75 = \frac{R_3}{R_2} (1.25)$$

$$R_3 = \frac{0.75}{1.25} \times 110.9 \text{ k}\Omega$$

$$R_3 = 66.54 \text{ k}\Omega$$

After tuning:-

$$R_1 = 12 \text{ k}\Omega$$

$$R_2 = 111.2 \text{ k}\Omega$$

$$R_3 = 68 \text{ k}\Omega$$